

Lab 2 Report - Design and Simulation of ALU with sequential machine controlled datapath

Lab Targets

Design an 8-bit Arithmetic Logical Unit (ALU), based on the method of top-down module system design.

Use the simple ALU from the previous experiment and write other circuits to complete the circuit design and test code writing. Under the EDA platform - ModelSim, complete the design input, compilation, and functional simulation verification.


Circuit Diagram

Steps to Generate Circuit Diagram

Step1: Processing > start > Analysis & Elaboration

Step2: Tools > Netlist viewer > RTL viewer

Diagram

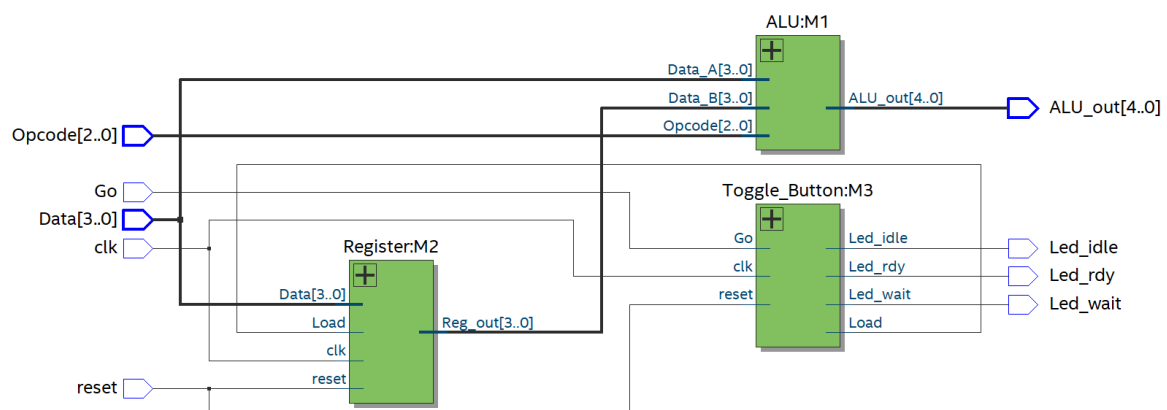

Code and Comments

Top Model - Lab2.v

```
1 module Lab2 (  
2     output [4:0] ALU_out,  
3     output Led_idle, Led_wait, Led_rdy,  
4     input [3:0] Data,  
5     input [2:0] Opcode,  
6     input Go,  
7     input clk,reset  
8 );  
9     wire [3:0] Reg_out;  
10  
11     ALU          M1 (ALU_out, Data, Reg_out, Opcode);  
12     Register     M2 (Reg_out, Data, Load, clk, reset);  
13     Toggle_Button M3 (Load, Led_idle, Led_wait, Led_rdy, Go, clk, reset);  
14  
15 endmodule
```

This model named Lab1, has five input port and four output ports. Which are

1. ALU_out: A 5-bit output, which is result of number after ALU process.
2. Led_idle, Led_wait, Led_rdy: These three are LED to indicate the internal status of the system.
3. Data: A 4-bit input, the data be sent to ALU.
4. Opcode: A 3-bit input, to control the ALU function.
5. Go: It is a button to control the system.
6. clk: A clock signal.
7. reset: Hardware reset.

ALU - Lab1.v

This part using the same design in Lab 1.

Register - Register.v

```
1 module Register (output reg [3:0] Reg_out, input [3:0] Data, input Load, clk, reset);  
2     always @(posedge clk) begin  
3  
4         if(reset) Reg_out = 4'b0;  
5         else begin  
6             if(Load) Reg_out <= Data ;  
7         end  
8     end  
9 endmodule
```

This model named Register. Having 5 ports.

1. Reg_out: One 4-bit register type output, sending the data to ALU model.
2. Data: One 4-bit input, sending the data in the register.
3. Load: When **load** is HIGH, the data can write into the register. When load is LOW, the data can read out of the register.
4. clk: Clock signal.
5. reset: When **reset** is HIGH, the content of the register should be empty.

Line 2: Statement `always` here to tell that the following codes always at the positive edges of the clock signal, clk.

Line 4: If **reset** signal is HIGH, then clears the register. In our implementation, sending zero to output directly.

Line 5 to Line 7: If **reset** signal is LOW and **Load** signal is HIGH, sending input data to Reg_out. According to behavior of Register model are controlled by clock, the data will keeping in one clock cycle.

Toggle Bottom - Toggle_Bottom.v


```
1  module Toggle_Button (output reg Load, Led_idle, Led_wait, Led_rdy, input Go, clk, reset);
2      reg [1:0] state = 0;
3
4      always @(posedge clk) begin
5
6          if(reset) state = 0;
7          else begin
8              if(Go && state == 0) state = 2'b1;
9              else if(state == 1) state = 2'b10;
10             else if(!Go && state == 2'b10) state = 2'b11;
11             else if (Go && state == 2'b11) begin
12                 state = 2'b1;
13                 Led_rdy = 0;
14             end
15         end
16
17         case(state)
18             2'b0:          begin
19                             Led_idle = 1;
20                             Led_wait = 0;
21                             Led_rdy = 0;
22                             Load = 0;
23                         end
24
25             2'b1:          begin
26                             Led_idle = 0;
27                             Load = 1;
28                         end
29
30             2'b10:         begin
31                             Load = 0;
32                             Led_wait = 1;
33                         end
34
35             2'b11:         begin
36                             Led_wait = 0;
37                             Led_rdy = 1;
38                         end
39         endcase
40     end
41 endmodule
```

This model named Register. Having 7 ports,

1. Load: One bit register type output, using for register model.
2. Led_idel, Led_wait, Led_rdy: These three are LED to indicate the internal status of the system.
3. Go: It is a button to control the system.

4. clk: Clock signal.
5. reset: When **reset** is HIGH, this model go to idle.

The following is flow chart of this model

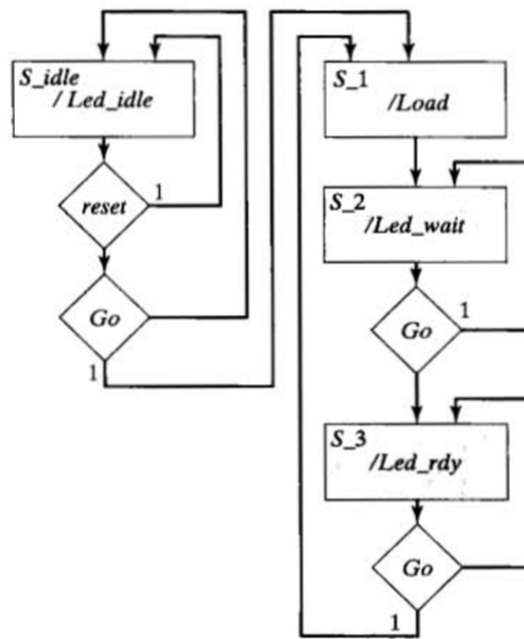

Line 6: If **reset** signal is HIGH, the state of this model goes to initial state - **S_idle**. In our code, it is state 0.

Line 7 to Line 14: This part we using `if...else...` statements to control the state of this model, the state are following the above ASM chart.

Line 17 to Line 39: This part is a `case` statement. Cooperating with state register in Line 2. For each state, this part statements used for control output ports.

Testbench and Wave

Testbench - Lab2.vt

```

1  module Lab2_vlg_tst();
2  // constants
3  // general purpose registers
4  reg eachvec;
5  // test vector input registers
6  reg [3:0] Data;
7  reg Go;
8  reg [2:0] Opcode;
9  reg clk;
10 reg reset;
11 reg count;
12 // wires
13 wire [4:0] ALU_out;
14 wire Led_idle;
15 wire Led_rdy;
16 wire Led_wait;
17
18 // assign statements (if any)
19 Lab2 i1 (


```

```


20 // port map - connection between master ports and signals/registers
21     .ALU_out(ALU_out),
22     .Data(Data),
23     .Go(Go),
24     .Led_idle(Led_idle),
25     .Led_rdy(Led_rdy),
26     .Led_wait(Led_wait),
27     .Opcode(Opcode),
28     .clk(clk),
29     .reset(reset)
30 );
31 initial
32 begin
33 // code that executes only once
34 // insert code here --> begin
35
36     clk = 0;
37
38     Go = 0;
39     reset =0;
40     Data = 4'b0;
41     Opcode = 3'b0;
42
43     forever #5 clk = ~clk;
44
45 // --> end
46 $display("Running testbench");
47 end
48
49 initial begin
50 #200 reset = 1;
51 #13 reset = 0;
52 end
53
54
55 always
56 // optional sensitivity list
57 // @(event1 or event2 or .... eventn)
58 begin
59 // code executes for every event on sensitivity list
60 // insert code here --> begin
61
62 for(count = 3'b0 ; count<= 3'b111 ;count = count+1)
63     begin
64         Data = 4'b0010;
65         #3 Go = 1;
66         #50 Go = 0;
67         #10 Opcode= Opcode + 1;
68     end
69
70 @eachvec;
71 // --> end
72 end
73 endmodule

```

Wave

 

 We using one operation explain in detail.



From the above figure we can see that **Data** is 0010, **Reg_out** which is last data in register is 0010, and **Opcode** is 001 which function is subtract.


When **Go** signal is HIGH, in the next clock, **Led_rdy** from HIGH to LOW, at the same time, **Load** is from LOW to HIGH, to control the register store the data.

After next clock, **Load** signal becomes LOW, and **Led_wait** becomes HIGH, it is meaning the system is waiting to start calculate.

$$0010_2 - 0010_2 = 00000_2$$

We can seen the output is 00000, it is correct.

Reset function

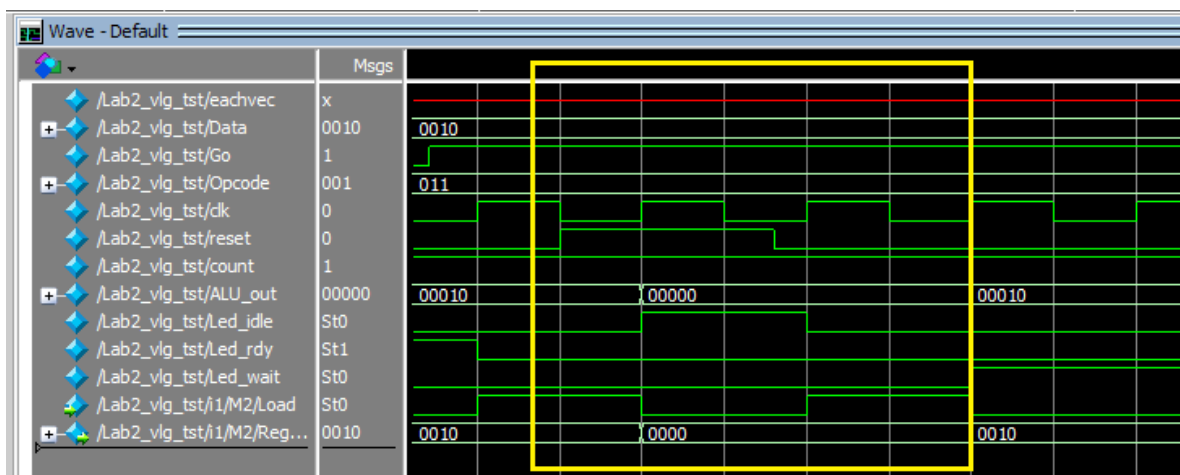

From the wave figure we can seen after **reset** is HIGH, in next positive edge of clock, **Reg_out** is 0000, **Load** is LOW, **Led_idle** is HIGH, and **ALU_out** is 00000.

This result is our expected.