

# 《数字系统设计》实验报告

## 8 位简单算逻运算单元电路设计

### 8-bit Simple ALU

小组成员（按姓氏首字母排序）：

姓名	UCD 学号	北工大学号
CHEN DINGRUI	17206208	17371131
GONG CHEN	17205914	17371117
LIU ZIYANG	16206553	16371322
SHI BO	17205870	17374120
XU ZHIKUN	17205897	17371130
ZHU YANXING	17205900	17371118

评语及分项得分

分项	实验预习及 实验方案	出勤	实验结果 及分析	现场问答	实验报告
评语					
得分					

最终评定得分：\_\_\_\_\_

2019 年 12 月 10 日

# Lab 1 Report - 8-bit Simple ALU

## Lab 1 Report - 8-bit Simple ALU

Lab Targets

Circuit Diagram

Steps to Generate Circuit Diagram

Diagram

Code and Comments

ALU - Lab1.v

Testbench and Wave

Testbench - Lab1.vt

Wave

Resource Allocation

Summary

## Source Code

ALU - Lab1.v

ALU Test Bench

## Lab Targets

Design an 8-bit Arithmetic Logical Unit (ALU), based on the method of top-down module system design.

The functions are shown in the table, and eight operations such as addition, subtraction, logical AND, and OR are implemented according to the operation code.

The input operand is an 8421 code combination corresponding to a four-digit number starting from the end of the student number.

Operand	Function
Add	$a + b$
Subtract	$a - b$
Or_AB	$a \mid b$
And_AB	$a \& b$
Not A	$\sim a$
Exor	$a \wedge b$
Exnor	$a \sim \wedge b$
Ror_A	$\mid a$


## Circuit Diagram

### Steps to Generate Circuit Diagram

Step1: Processing > start > Analysis & Elaboration

Step2: Tools > Netlist viewer > RTL viewer

## Diagram

 

## Code and Comments

### ALU - Lab1.v

```
1 module Lab1(output reg [7:0] ALU_out, input [7:0] Data_A, Data_B, input [2:0] Opcode);
2     parameter    Add      = 3'b000,    // A + B
3                 Subtract  = 3'b001,    // A - B
4                 Or_AB     = 3'b010,    // A | B
5                 And_AB    = 3'b011,    // A & B
6                 Not_A     = 3'b100,    // ~ A
7                 Exor      = 3'b101,    // A ^ B
8                 Exnor     = 3'b110,    // A ~ ^ B
9                 Ror_A     = 3'b111;    // | A
10
11     always@(*)
12
13     case(Opcode)
14         Add:      ALU_out = Data_A + Data_B;
15         Subtract: ALU_out = Data_A - Data_B;
16         Or_AB:    ALU_out = Data_A | Data_B;
17         And_AB:   ALU_out = Data_A & Data_B;
18         Not_A:    ALU_out = ~ Data_A;
19         Exor:     ALU_out = Data_A ^ Data_B;
20         Exnor:    ALU_out = Data_A ~^ Data_B;
21         Ror_A:    ALU_out <= {Data_A[0],Data_A[7:1]};
22     endcase
23 endmodule
```

This model named Lab1, has one input port and three output ports. Which are

1. ALU\_out: A 8-bit output, which is result of number after ALU process.
2. Data\_A: A 8-bit input, the first data be sent to ALU.
3. Data\_B: A 8-bit input, the second data be sent to ALU.
4. Opcode: A 3-bit input, to control the ALU function.

We declare 8 parameters for identifying 8 operations respectively. The details are described in the following table.

Operation	Function	Opcode	Operation	Function	Opcode
Add	$a + b$	000	Not A	$\sim a$	100
Subtract	$a - b$	001	Exor	$a \wedge b$	101
Or_AB	$a   b$	010	Exnor	$a \sim \wedge b$	110
And_AB	$a \& b$	011	Ror_A	$  a$	111

---

In line 11, `always@(*)` statement *always* here to tell that the following codes always run.

Start at line 13 is case statement, which is used to define the functions of each operation in details.

## Testbench and Wave

### Testbench - Lab1.vt

```
1  module Lab1_vlg_tst();
2  // test vector input registers
3  reg [7:0] Data_A;
4  reg [7:0] Data_B;
5  reg [2:0] Opcode;
6  // wires
7  wire [7:0] ALU_out;
8
9  // assign statements (if any)
10 Lab1 i1 (
11 // port map - connection between master ports and signals/registers
12     .ALU_out(ALU_out),
13     .Data_A(Data_A),
14     .Data_B(Data_B),
15     .Opcode(Opcode)
16 );
17 initial
18 begin
19 // code that executes only once
20 // insert code here --> begin
21     Data_A = 8'b00100011;
22     Data_B = 8'b00111000;
23
24     #20 Opcode = 3'b000;
25     #20 Opcode = 3'b001;
26     #20 Opcode = 3'b010;
27     #20 Opcode = 3'b011;
28     #20 Opcode = 3'b100;
29     #20 Opcode = 3'b101;
30     #20 Opcode = 3'b110;
31     #20 Opcode = 3'b111;
32 // --> end
33 $display("Running testbench");
34 end
35 endmodule
```

From *Experiments Handbook of Digital System Design* we know that the input operand is an 8421 code combination corresponding to a four-digit number starting from the end of the student number.


In this testbench, we use Student Number is 16206553, so the input number are  $35_{10}$  and  $56_{10}$

$$35_{10} = 00100011_2$$

$$56_{10} = 00111000_2$$

Then, we tested each opcode every 20 ps.

## Wave

 

We can see the output result are we expected.

## Resource Allocation

Shi Bo: All the Lab 1 is finished by Shi Bo.

## Summary

In this Lab, our team designed a simple 8-bit ALU. Each of us participated in the experiment, completed the experiment together, and performed a simulation test. We successfully completed this experiment and the results are satisfactory.

## Source Code

### ALU - Lab1.v

```
1 module Lab1(output reg [7:0] ALU_out, input [7:0] Data_A, Data_B, input [2:0] Opcode);
2     parameter Add = 3'b000, // A + B
3             Subtract = 3'b001, // A - B
4             Or_AB = 3'b010, // A | B
5             And_AB = 3'b011, // A & B
6             Not_A = 3'b100, // ~ A
7             Exor = 3'b101, // A ^ B
8             Exnor = 3'b110, // A ~ ^ B
9             Ror_A = 3'b111; // | A
10
11     always@(*)
12
13     case(Opcode)
14         Add: ALU_out = Data_A + Data_B;
15         Subtract: ALU_out = Data_A - Data_B;
16         Or_AB: ALU_out = Data_A | Data_B;
17         And_AB: ALU_out = Data_A & Data_B;
18         Not_A: ALU_out = ~ Data_A;
19         Exor: ALU_out = Data_A ^ Data_B;
20         Exnor: ALU_out = Data_A ~^ Data_B;
21         Ror_A: ALU_out <= {Data_A[0],Data_A[7:1]};
22     endcase
23 endmodule
```

# ALU Test Bench

```
1 // Copyright (C) 2018 Intel Corporation. All rights reserved.
2 // Your use of Intel Corporation's design tools, logic functions
3 // and other software and tools, and its AMPP partner logic
4 // functions, and any output files from any of the foregoing
5 // (including device programming or simulation files), and any
6 // associated documentation or information are expressly subject
7 // to the terms and conditions of the Intel Program License
8 // Subscription Agreement, the Intel Quartus Prime License Agreement,
9 // the Intel FPGA IP License Agreement, or other applicable license
10 // agreement, including, without limitation, that your use is for
11 // the sole purpose of programming logic devices manufactured by
12 // Intel and sold by Intel or its authorized distributors. Please
13 // refer to the applicable agreement for further details.
14
15 // *****
16 // This file contains a Verilog test bench template that is freely editable to
17 // suit user's needs .Comments are provided in each section to help the user
18 // fill out necessary details.
19 // *****
20 // Generated on "10/25/2019 18:04:54"
21
22 // Verilog Test Bench template for design : Lab1
23 //
24 // Simulation tool : ModelSim-Altera (Verilog)
25 //
26 // *****
27 // My UCD Student Number is 16206553
28 // The input number are 35d and 56d.
29 // 0010 0011b and 0011 1000b.
30 // *****
31
32 `timescale 1 ps/ 1 ps
33 module Lab1_vlg_tst();
34 // constants
35 // general purpose registers
36 reg eachvec;
37 // test vector input registers
38 reg [7:0] Data_A;
39 reg [7:0] Data_B;
40 reg [2:0] Opcode;
41 // wires
42 wire [7:0] ALU_out;
43
44 // assign statements (if any)
45 Lab1 i1 (
46 // port map - connection between master ports and signals/registers
47     .ALU_out(ALU_out),
48     .Data_A(Data_A),
49     .Data_B(Data_B),
50     .Opcode(Opcode)
51 );
```

```
52 initial
53 begin
54 // code that executes only once
55 // insert code here --> begin
56     Data_A = 8'b00100011;
57     Data_B = 8'b00111000;
58
59     #20 Opcode = 3'b000;
60     #20 Opcode = 3'b001;
61     #20 Opcode = 3'b010;
62     #20 Opcode = 3'b011;
63     #20 Opcode = 3'b100;
64     #20 Opcode = 3'b101;
65     #20 Opcode = 3'b110;
66     #20 Opcode = 3'b111;
67 // --> end
68 $display("Running testbench");
69 end
70 always
71 // optional sensitivity list
72 // @(event1 or event2 or .... eventn)
73 begin
74 // code executes for every event on sensitivity list
75 // insert code here --> begin
76
77 @eachvec;
78 // --> end
79 end
80 endmodule
81
```